

# Sequential Circuits

---

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Computer Science & Engineering, and

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.cse.iitb.ac.in/~viren/>

E-mail: viren@{cse, ee}.iitb.ac.in


*CS-230: Digital Logic Design & Computer Architecture*

---



Lecture 16 (10 February 2022)

**CADSL**

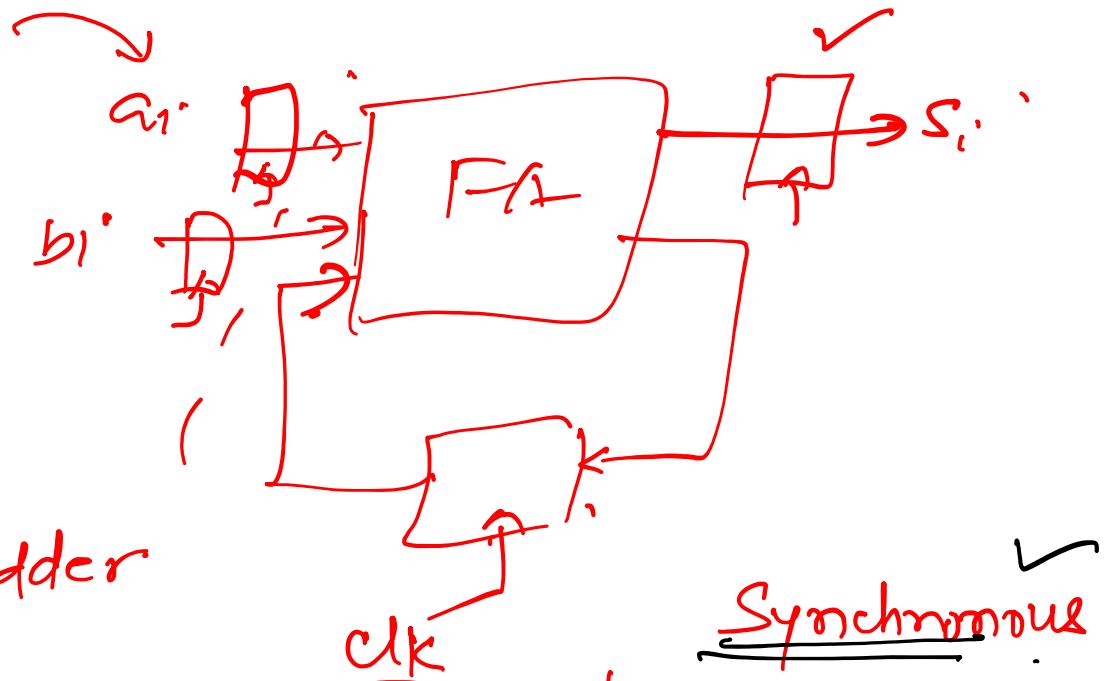


Parallel Adder

↓  
serial adder



(Temporal) ✓

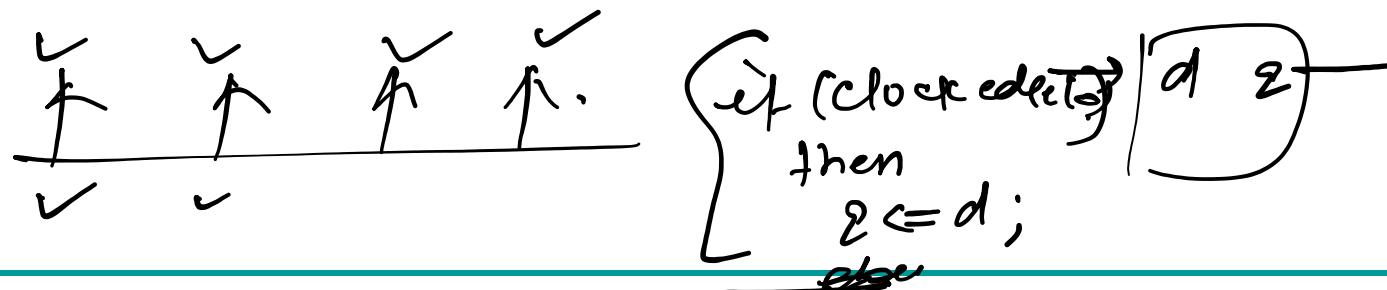✓  
Synchronous  
Sequential.  
Circuits .


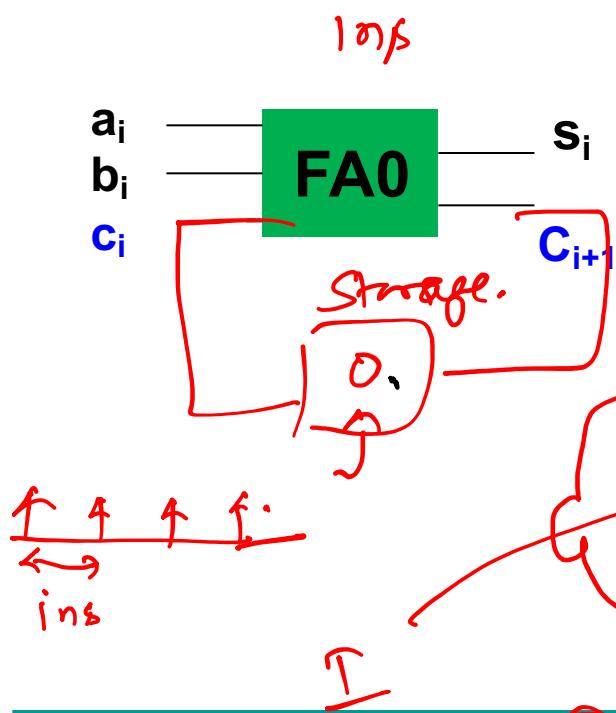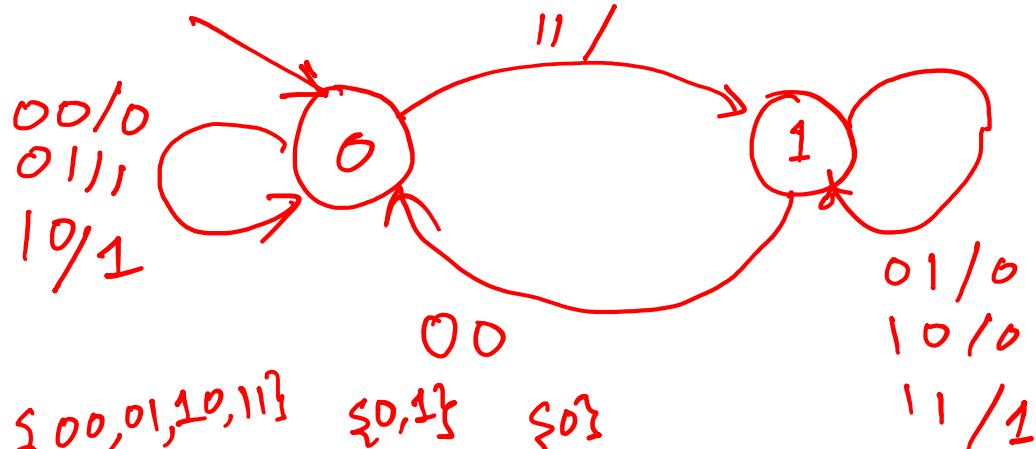
# Serial Adder


$$\begin{array}{r}
 c_{32} \ c_{31} \dots \ c_2 \ c_1 \ 0 \\
 a_{31} \dots \ a_2 \ a_1 \ a_0 \\
 + b_{31} \dots \ b_2 \ b_1 \ b_0 \\
 \hline
 s_{31} \dots \ s_2 \ s_1 \ s_0
 \end{array}$$




$$M(I, O, S, S_0, \delta, \lambda)$$

Annotations for the state transition function:

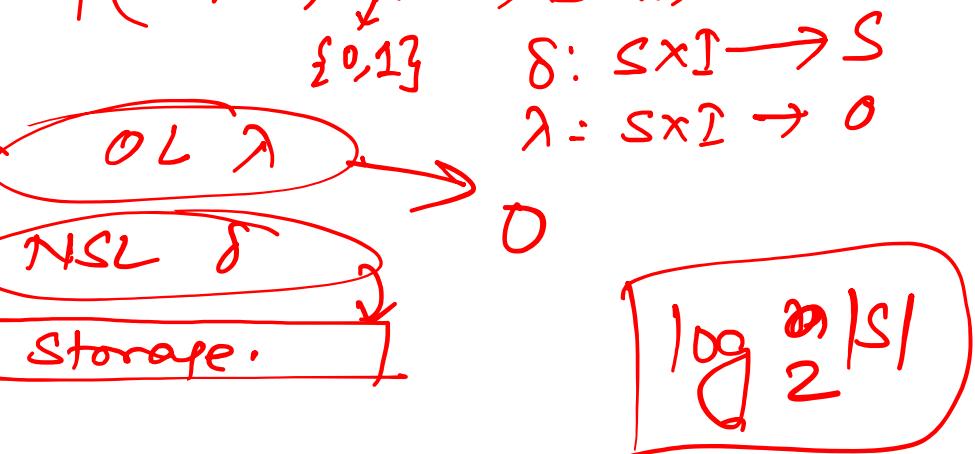- $\{00, 01, 10, 11\}$ ,  $\{0, 1\}$ ,  $\{0\}$
- $\{0, 1\}$
- $\delta: S \times I \rightarrow S$
- $\lambda: S \times I \rightarrow O$



# State Machine

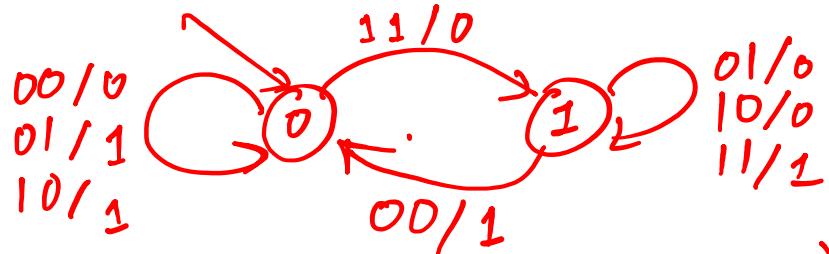

$$\delta = S \times I \rightarrow S$$

$\Delta$

		00	01	11	10
		0	0	1	0
		1	1	1	1
$\delta$					
0	0	0	1	0	1
1	1	1	1	0	1

$$= a \cdot b + \bar{a} \cdot b + \bar{a} \cdot a$$

$$I = \{ \underline{\underline{00}}, 01, 10, 11 \},$$

$a, b$

$$\delta(\underline{\underline{00}}, a, b)$$

$\delta$


		00	01	11	10
		0	1	0	1
		1	0	1	0
$\delta$					
0	0	0	1	0	1
1	1	1	0	1	0

$$\begin{aligned}
 \lambda &= \delta \cdot \bar{a} \bar{b} + \bar{\delta} \bar{a} b + \delta a b + \bar{\delta} a \bar{b} \\
 &= \delta \cdot (\bar{a} \bar{b} + a \cdot b) + \bar{\delta} \cdot (\bar{a} b + a \bar{b}) \\
 &= \delta \cdot (\bar{a} \oplus b) + \bar{\delta} \cdot (a \oplus b) \\
 &= 8 \oplus a \oplus b_4
 \end{aligned}$$

**CADSL**




# State Machine

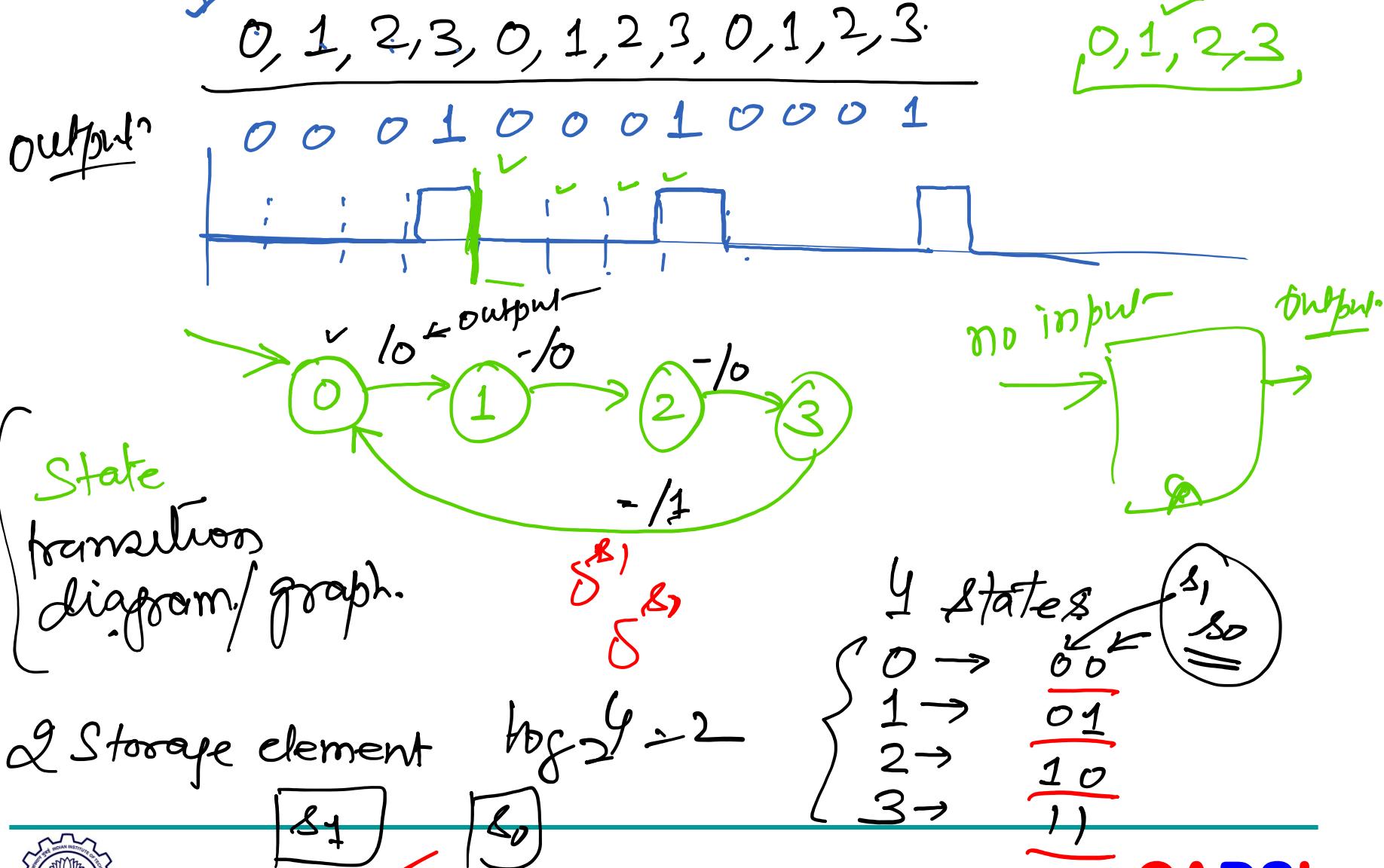

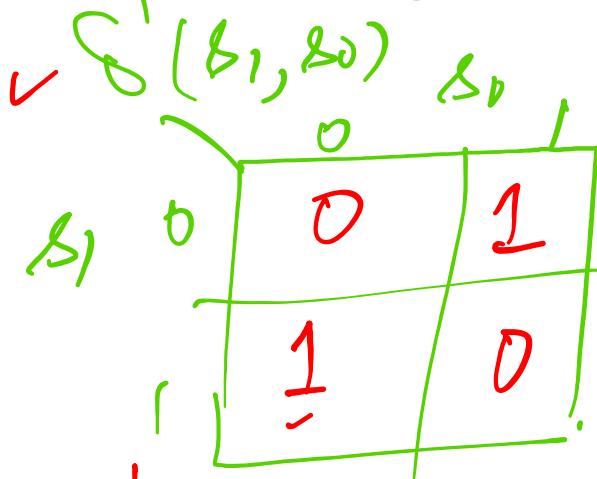
# Finite State Machine

$$\delta^1(S \times \Sigma \rightarrow S)$$




$$\delta(\delta, \delta_0)$$

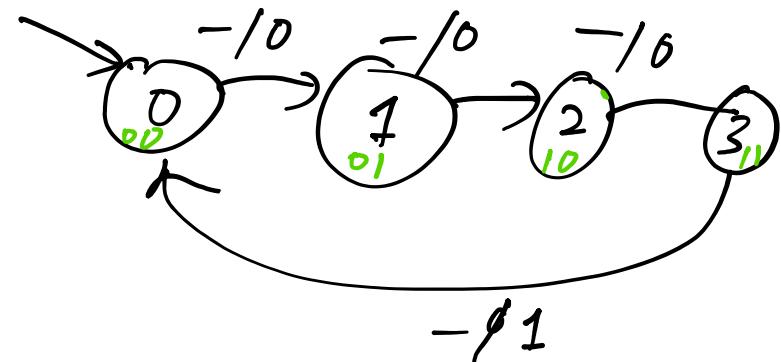


$$\delta^1(\delta_1, \delta_0) = \delta_1 \delta_0 + \delta_1 \delta_0$$
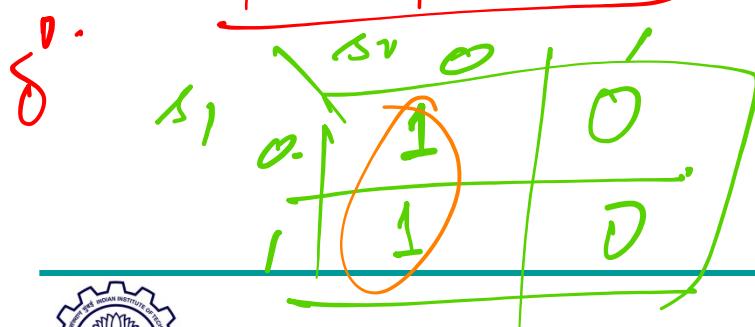
$$[\delta^1 = \delta_1 \oplus \delta_0]$$





$\delta^1(\delta_1, \delta_0) \leftarrow$  transition of  
 $\delta^0(\delta_1, \delta_0) \rightleftharpoons \delta_1$   
 transition of
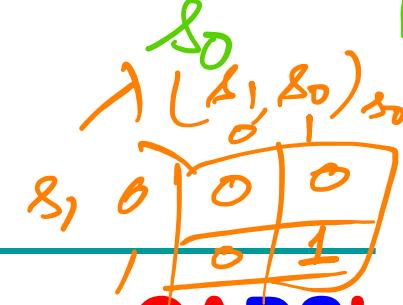
$$\delta^0(\delta_1, \delta_0) = \overline{\delta_0}$$



# Finite State Machine

temporal  
behaviours

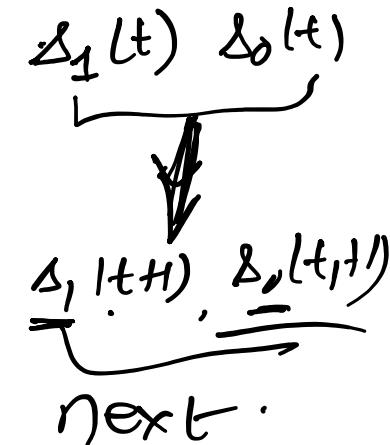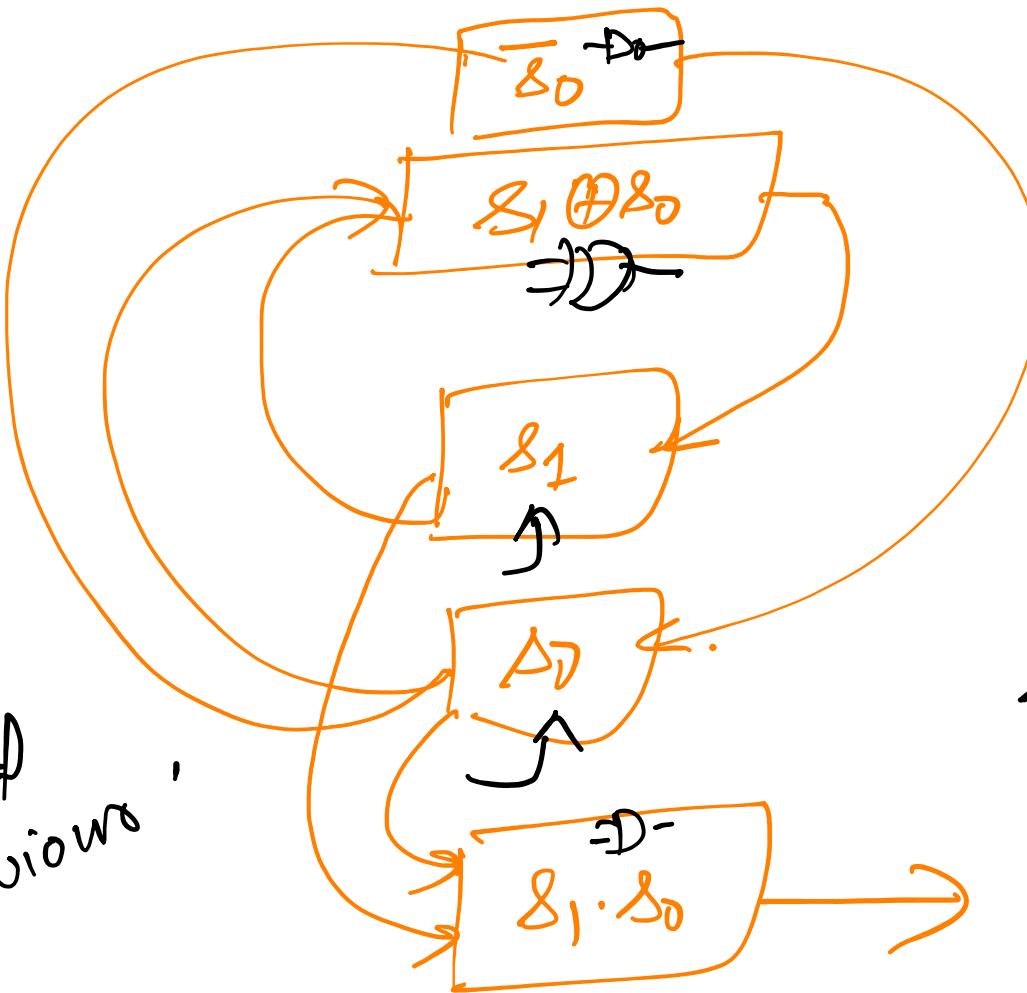

$$\underline{S_1(t+1)} = \underline{S_1(t)} \oplus \underline{S_0(t)}$$
$$\underline{S_0(t+1)} = \overline{\underline{S_0(t)}}$$





Output

$$\underline{\underline{O(t+1)}} = \underline{S_1(t+1)} \cdot \underline{S_0(t+1)}$$


CADSL



# Finite State Machine

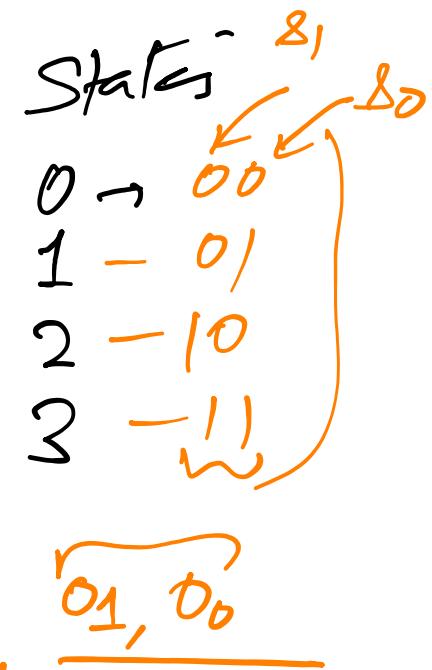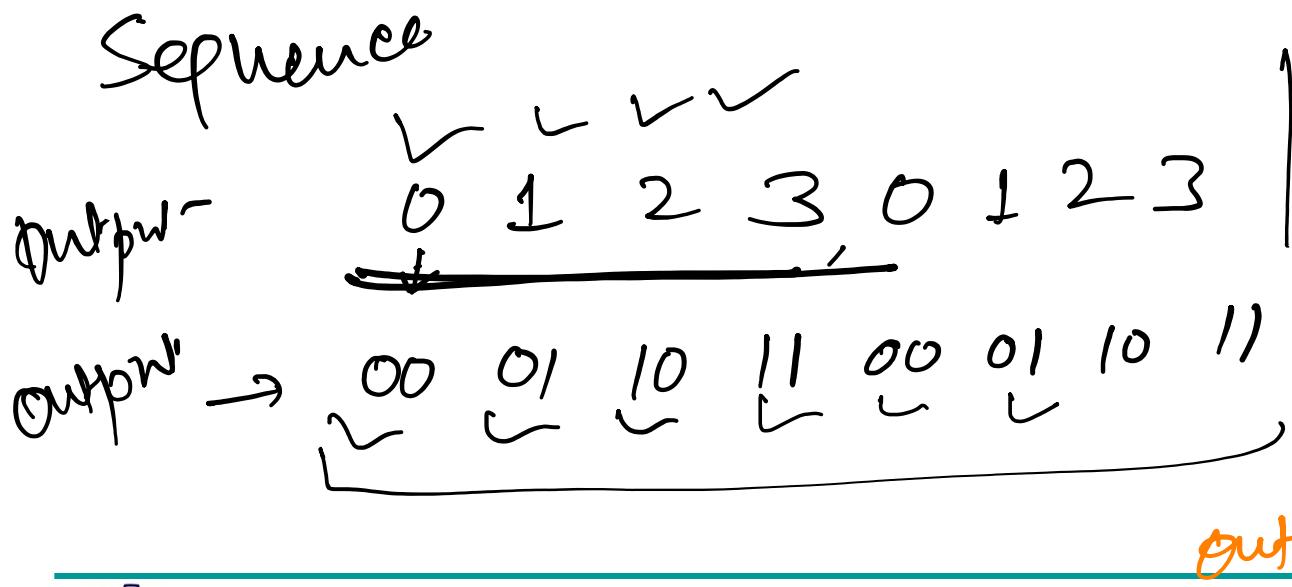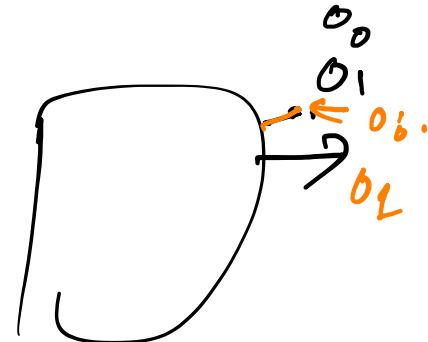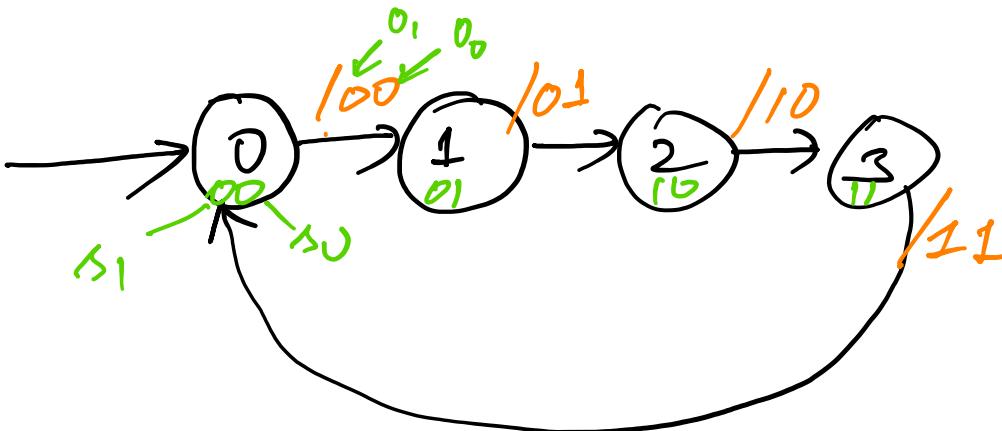

# Finite State Machine

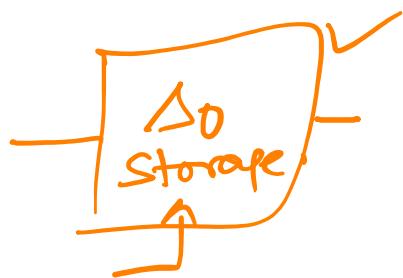

$\delta_1$	$\delta_0$
0	0
0	1
1	0
1	1

$$\begin{cases} \delta_1 \\ \delta_0 \end{cases} (\delta_1, \delta_0)$$

$$\begin{cases} \delta_1 \\ \delta_0 \end{cases} (\delta_1, \delta_0)$$



$$\begin{cases} \delta_1 \\ \delta_0 \end{cases} (\delta_1, \delta_0)$$



# Finite State machine

$$M(I, O, S, S_0, \delta, \lambda)$$
$$\delta: S \times I \rightarrow S$$
$$\lambda: S \times I \rightarrow O \leftarrow \text{Mealy machine}$$
$$\lambda: S \rightarrow O \leftarrow \text{Moore Machine.}$$

.

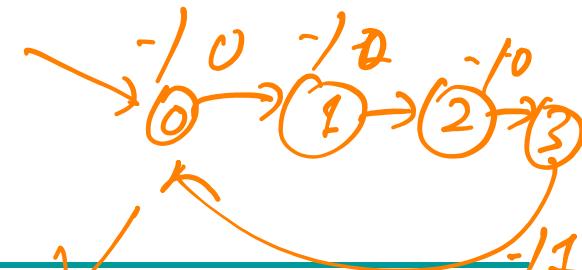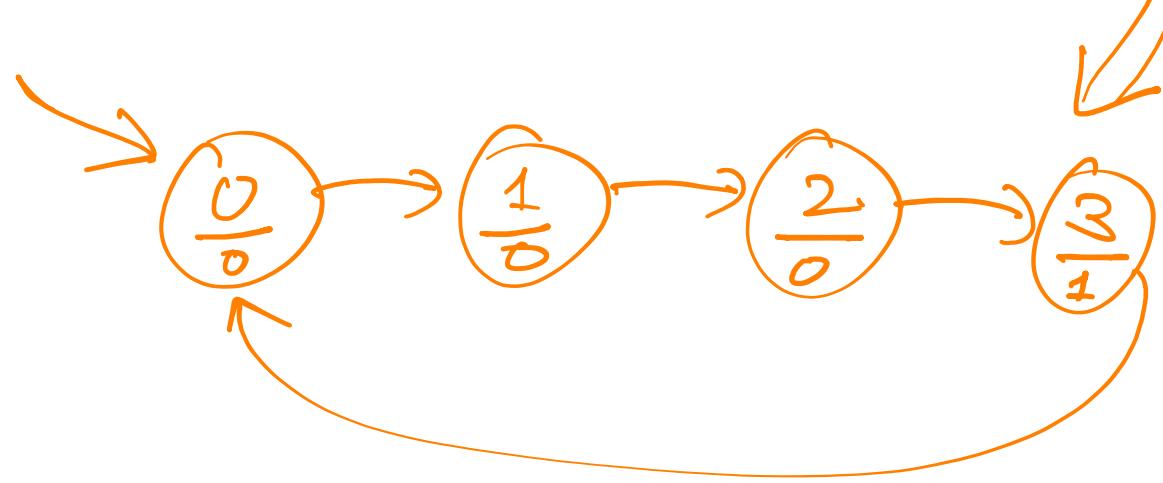


Mealy, machine CADSL



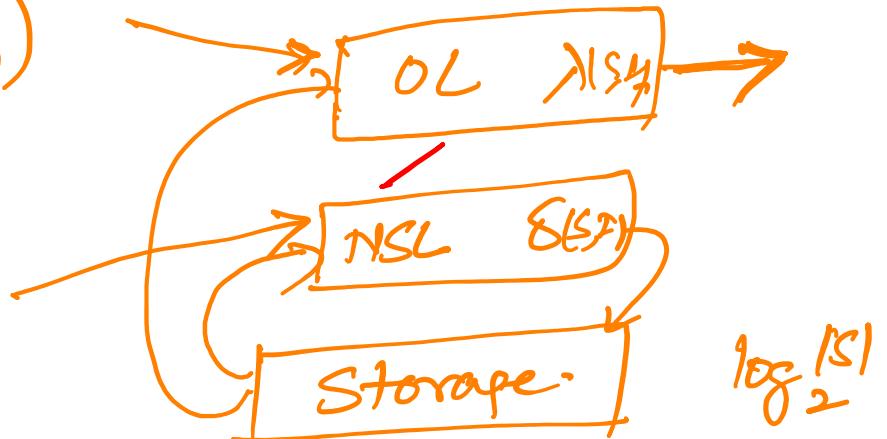
# Finite State machine

$$m(I, O, S, S_0, \delta, \lambda)$$

- How many storage elements
- encode the states
- Compute  $\delta$
- Compute  $\lambda$



Mealy m/c.

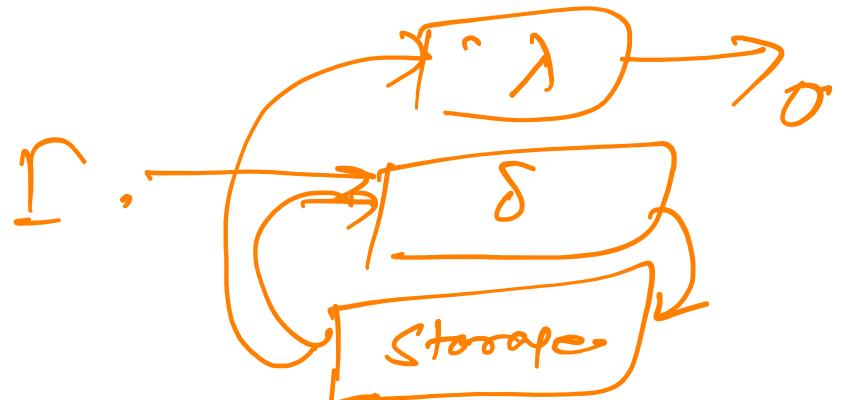

# Thank You

