

Logic: Implementation

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Computer Science & Engineering, and

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.cse.iitb.ac.in/~viren/>

E-mail: viren@cse, ee.iitb.ac.in


CS-230: Digital Logic Design & Computer Architecture



Lecture 6 (17 January 2022)

CADSL

Digital System

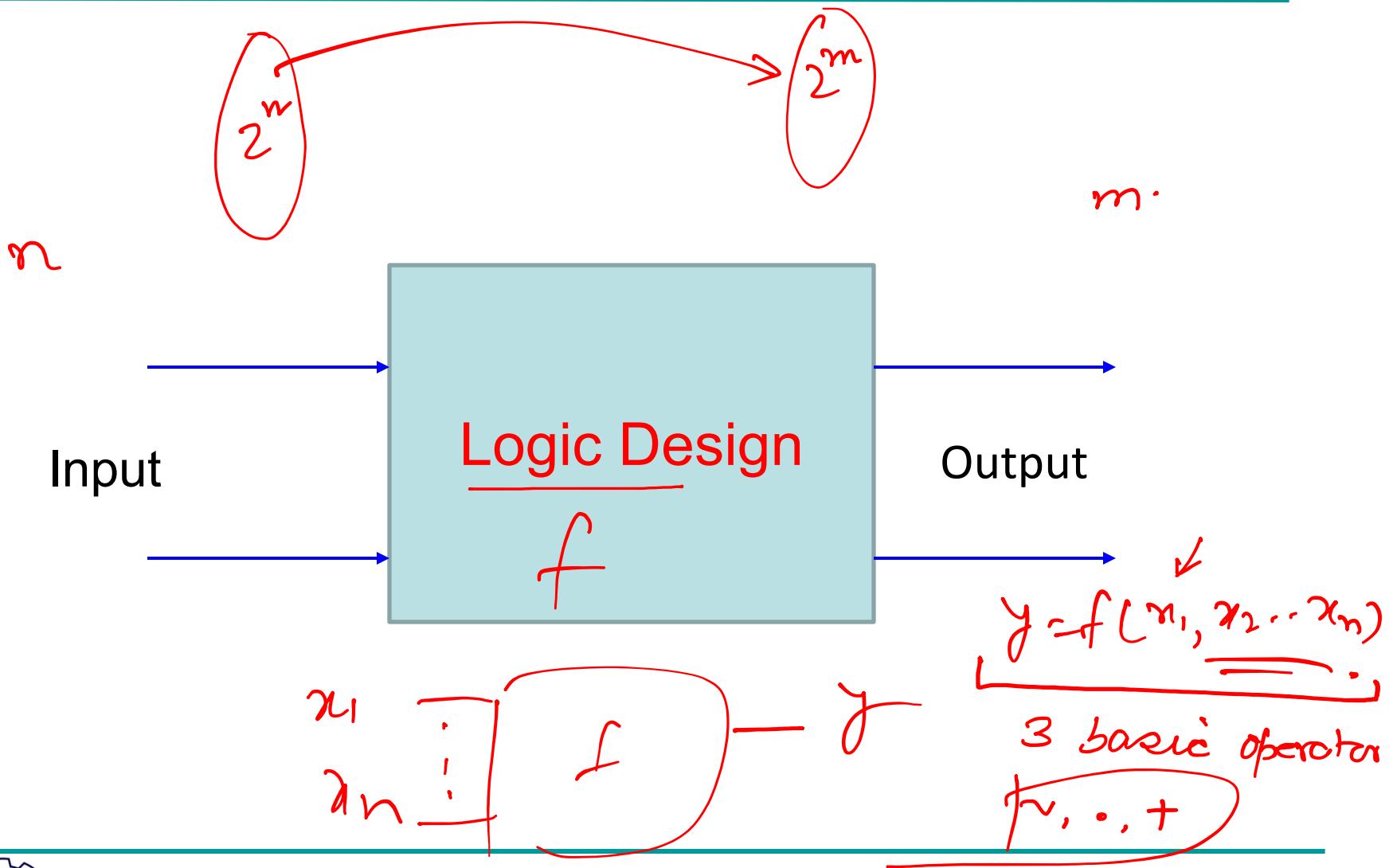


Minimum Operator Set

- Minimum number of operators
- $\{\sim, (+ \text{ or } .)\} / \{\neg, (\wedge \text{ or } \vee)\}$


Boolean
Algebra
DeMorgan's.

$$C = a \cdot b = \overline{(\overline{a} \cdot \overline{b})} \Rightarrow \overline{\overline{a} + \overline{b}}$$
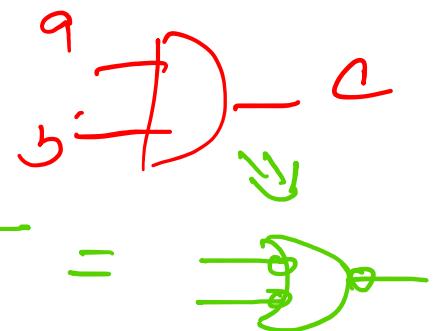
$$\overline{\overline{a} + \overline{b}}$$



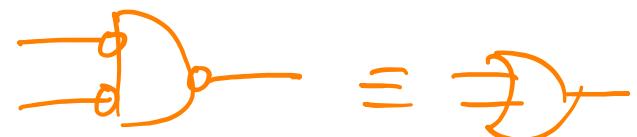
$$C = a + b = \overline{\overline{a} \cdot \overline{b}} = \overline{\overline{a} \cdot \overline{b}} = \overline{\overline{a} \cdot \overline{b}} = \overline{\overline{a} \cdot \overline{b}} = \overline{\overline{a} \cdot \overline{b}}$$



$\{\sim, \cdot\}$

$\{\sim, +\}$




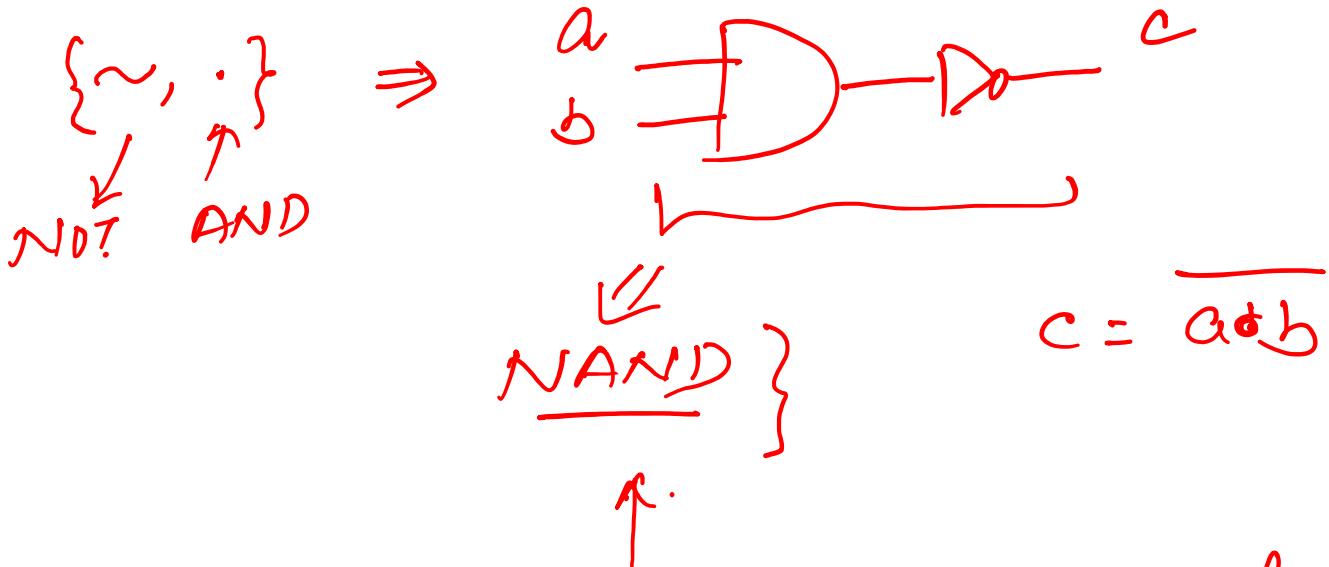


Can we represent any logical functions using only this operators

$$\{\sim, \cdot, +\}$$



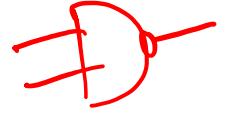

Universal Operator: NAND

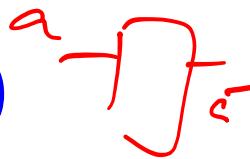

- NAND: Composite operator (AND and NOT)


- $\bar{a} = \overline{\underline{a} \cdot \underline{a}}$ \Rightarrow


- $a \cdot b = \overline{\underline{\underline{a}} \cdot \underline{\underline{b}}} = \overline{\underline{(a \cdot b)} \cdot \underline{(a \cdot b)}}$


- $a + b = \overline{\underline{\bar{a}} \cdot \underline{\bar{b}}} = \overline{\underline{(a \cdot a)} \cdot \underline{(b \cdot b)}}$



Universal Operator: NAND

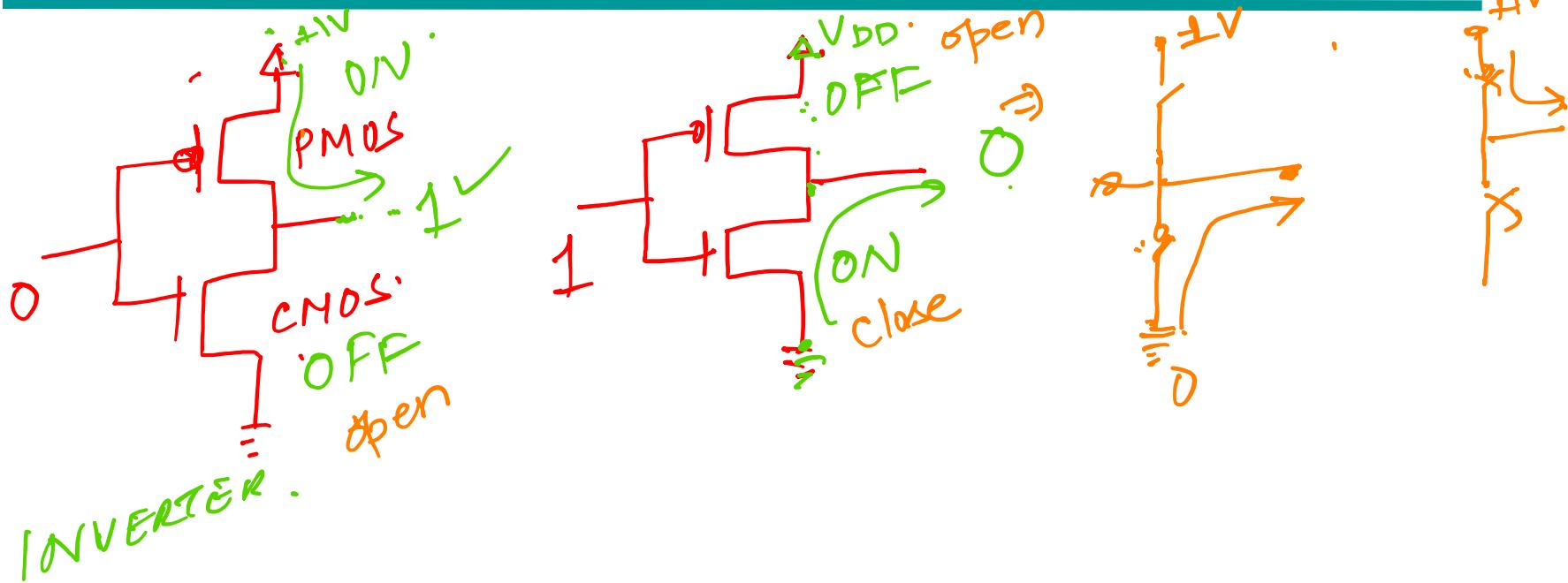

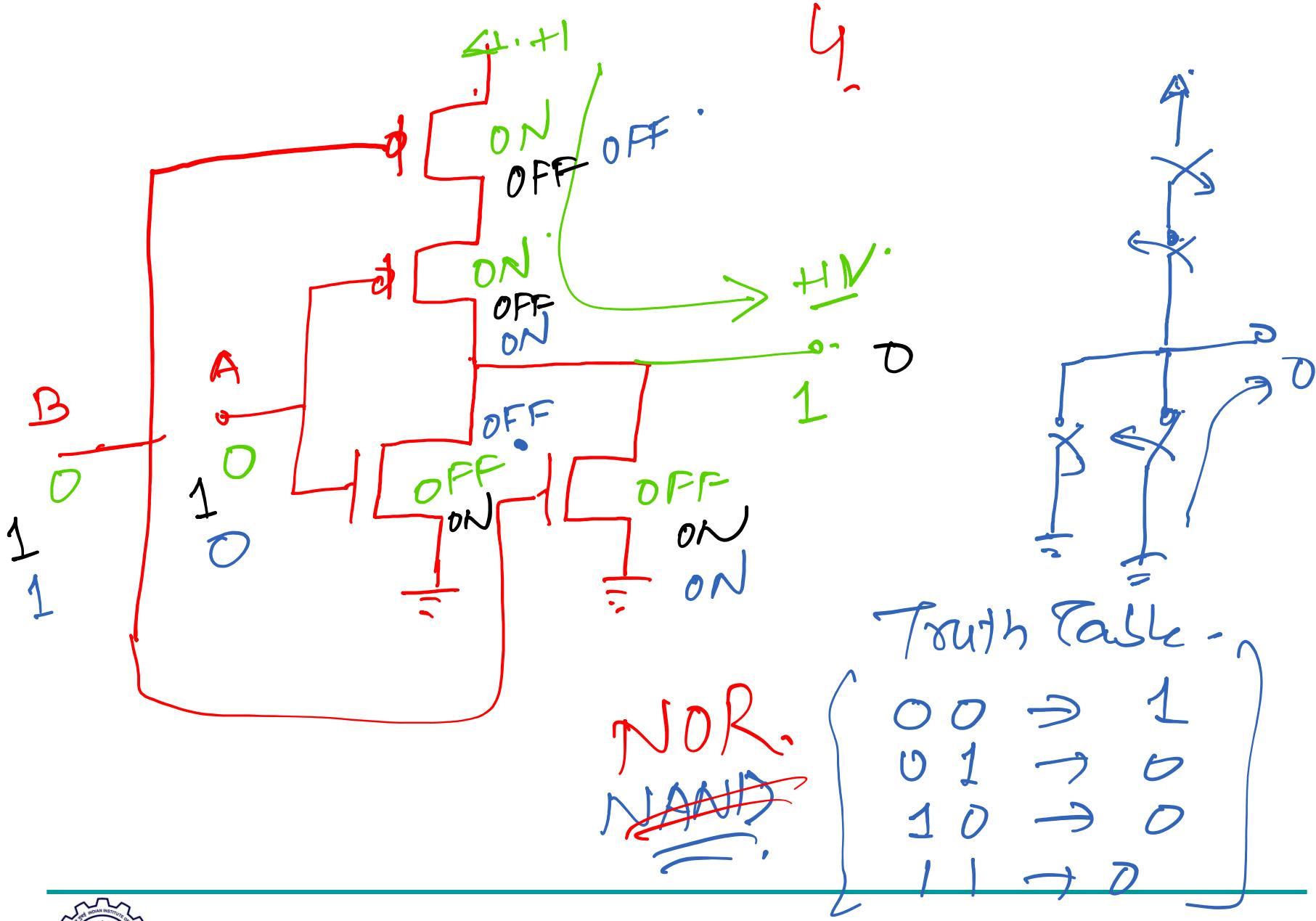

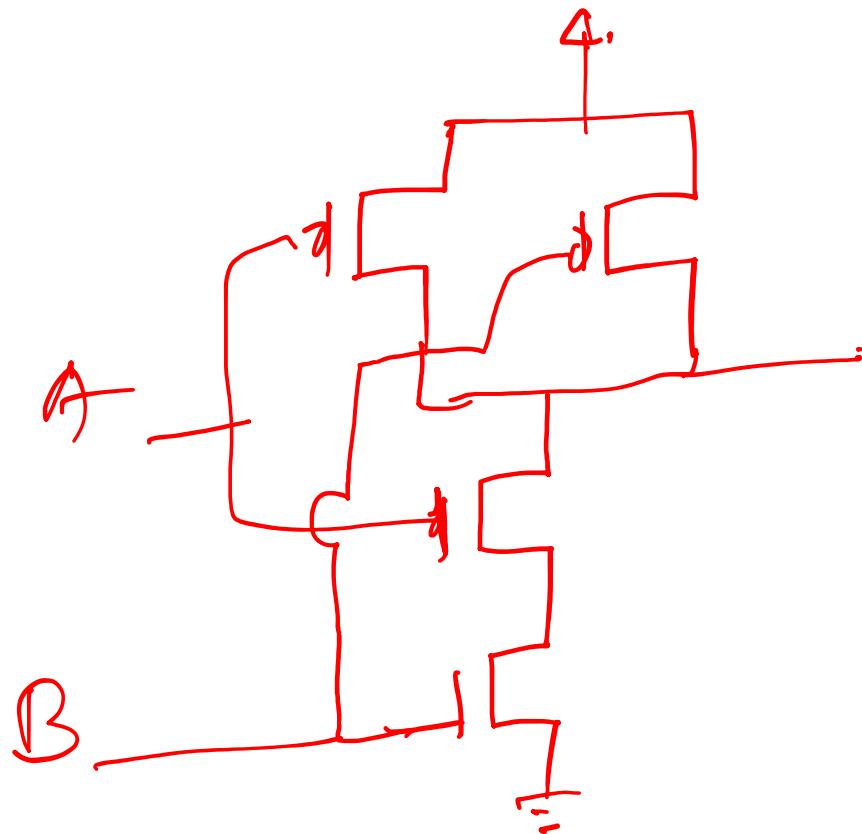

Y

2n

NAND

AND ·
NAND + NOT







Universal Operator: NOR $\{\sim, +\}$

- NOR: Composite operator (OR and NOT)


- $\overline{a} = \overline{a + a}$

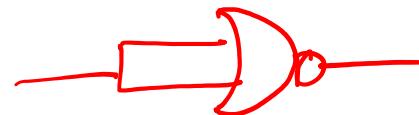

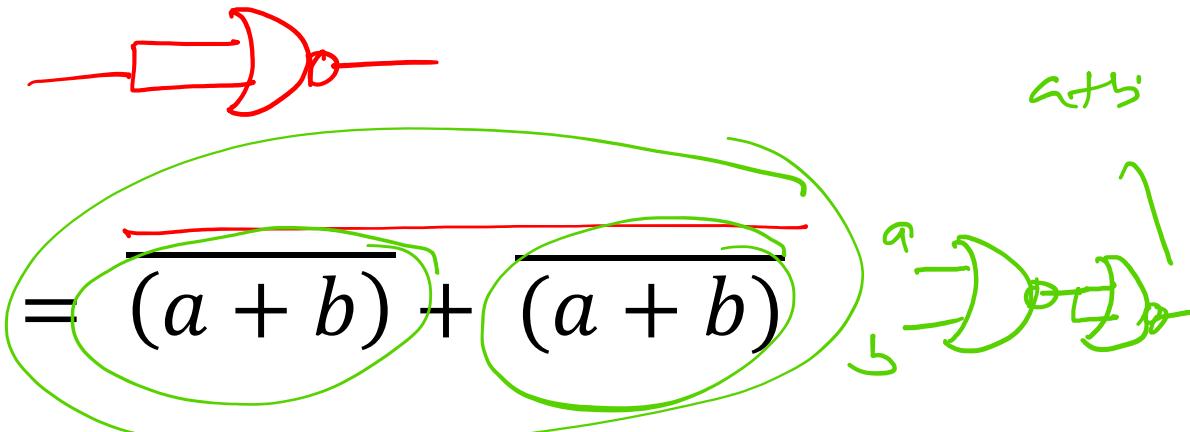
- $a + b = \overline{\overline{a + b}} = \overline{(a + b)} + \overline{(a + b)}$



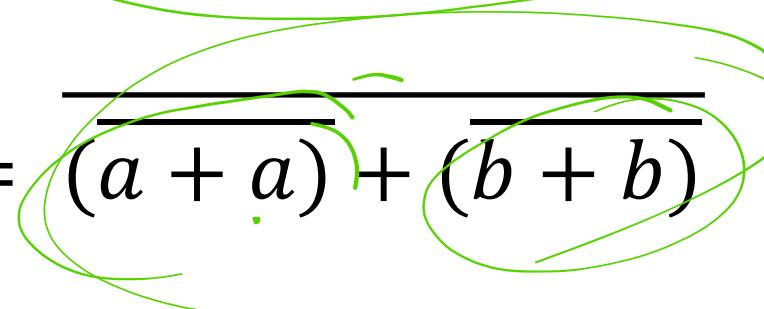- $a \cdot b = \overline{\overline{\overline{a + b}}} = \overline{\overline{(a + a)}} + \overline{\overline{(b + b)}}$



Universal Operator: NOR

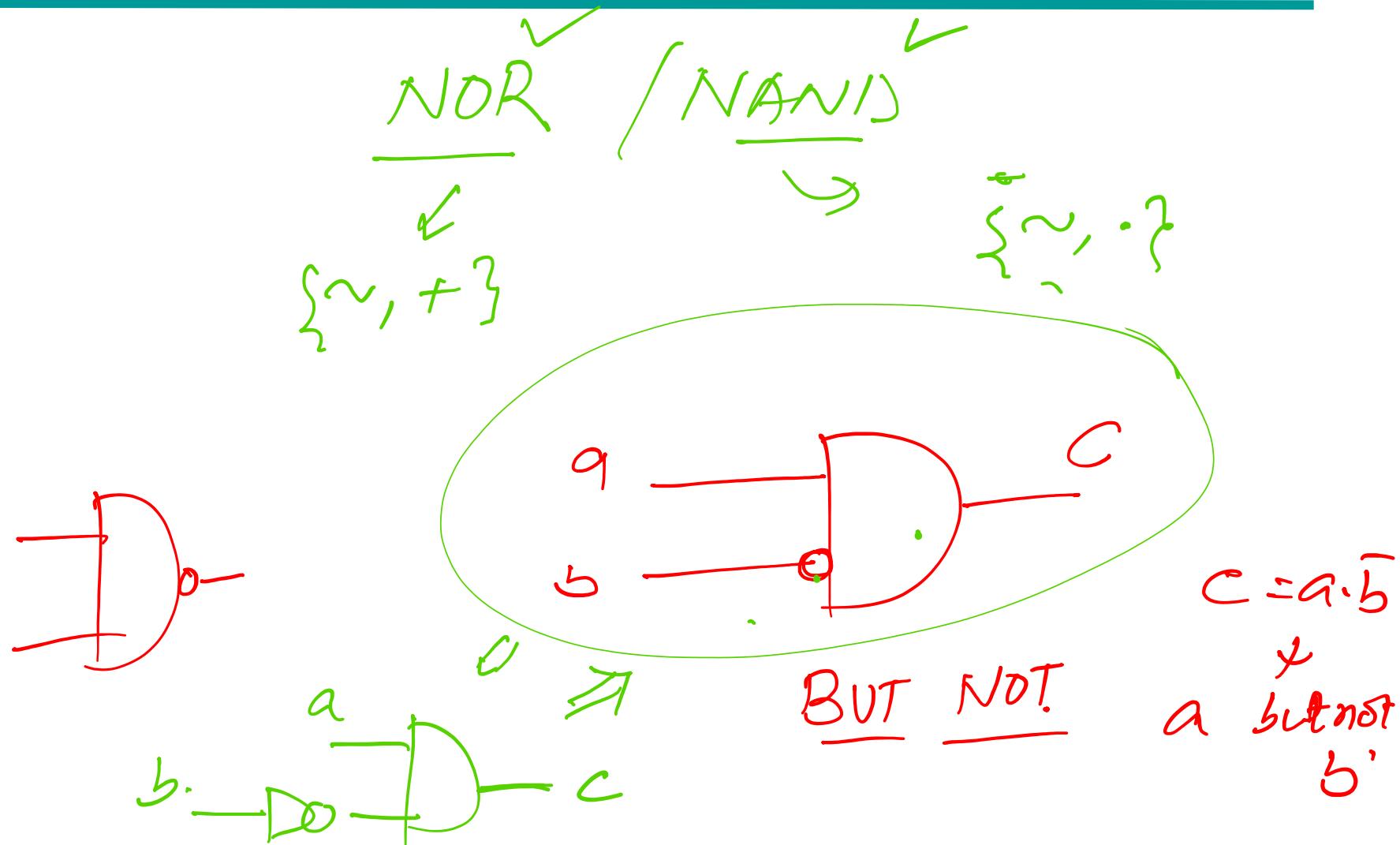

Complementing Functions

- Use DeMorgan's Theorem to complement a function:



1. Interchange AND and OR operators



2. Complement each constant value and literal

- Example: Complement $F = \overline{x.y.z} + x.\overline{y}.z$




$$\overline{F} = (\overline{x} + \overline{y} + z)(\overline{x} + y + z)$$



Logic Expression (SOP)

- $F = a \cdot b + c \cdot d$
- $\bar{F} = (\bar{a} + \bar{b}) \cdot (\bar{c} + \bar{d})$
- $\bar{\bar{F}} = F = (\bar{a} + \bar{b}) \cdot (\bar{c} + \bar{d})$
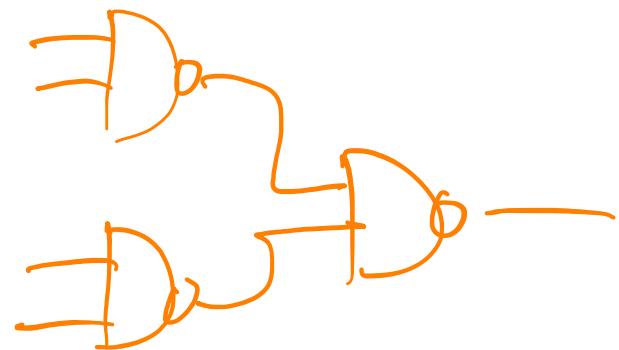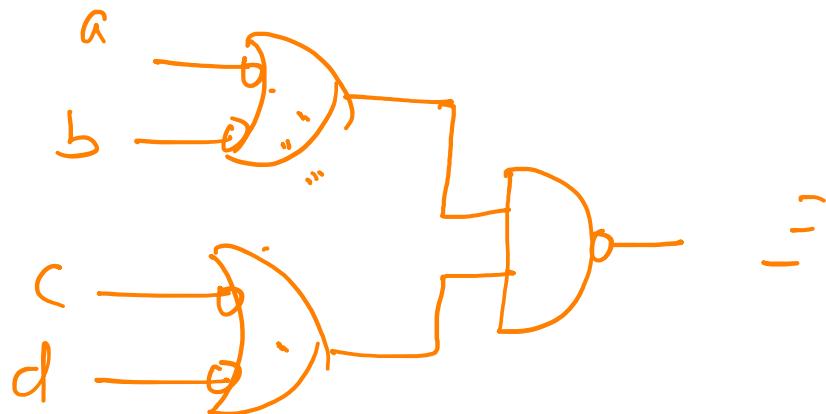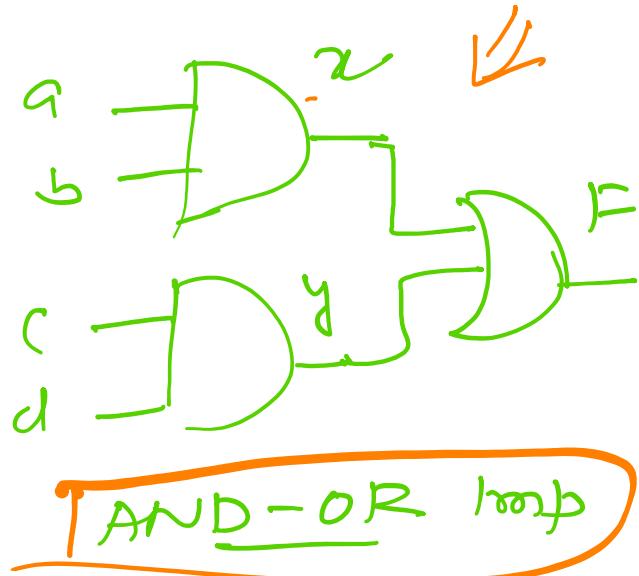
$$\bar{F} = \overline{a \cdot b + c \cdot d}$$
$$= (\bar{a} \cdot \bar{b}) \cdot (\bar{c} \cdot \bar{d})$$






Logic Expression (SOP)

- $F = a \cdot b + c \cdot d$
- $F = \overline{(\overline{a} + \overline{b}) \cdot (\overline{c} + \overline{d})}$



Logic Expression (POS)

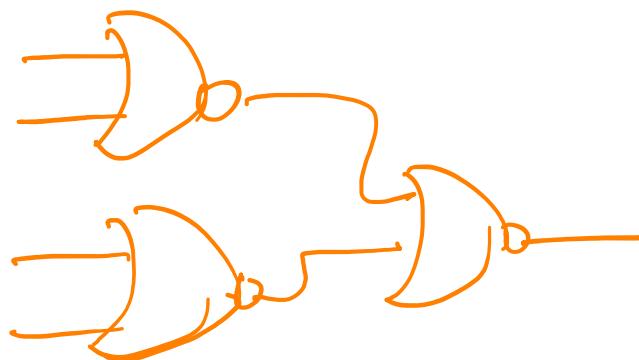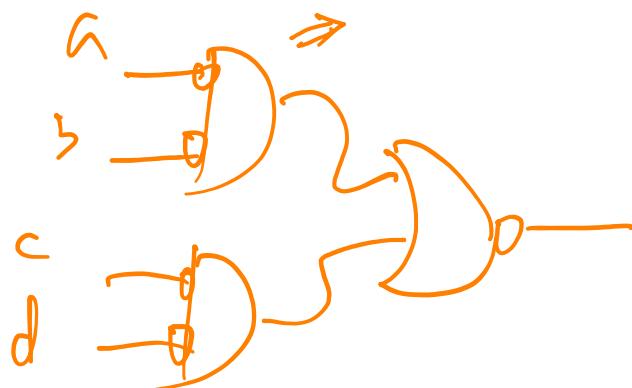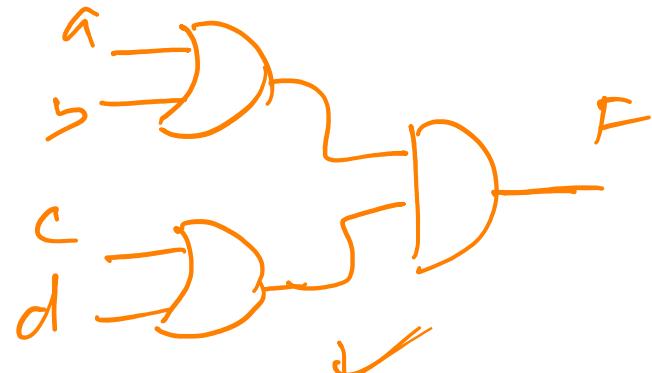- $F = (a + b) \cdot (c + d)$
- $\overline{F} = \overline{(a + b)} + \overline{(c + d)}$
- $\overline{F} = (\overline{a} \cdot \overline{b}) + (\overline{c} \cdot \overline{d})$
- $\overline{\overline{F}} = F = (\overline{a} \cdot \overline{b}) + (\overline{c} \cdot \overline{d})$



Logic Expression (POS)

- $F = (a + b) \cdot (c + d)$
- $F = \overline{(\overline{a} \cdot \overline{b})} + \overline{(\overline{c} \cdot \overline{d})}$



Truth Table

Truth Table

X	Y	Z	F
0	0	0	0
1	0	1	1
2	1	0	0
3	1	1	0
4	0	0	1
5	1	0	1
6	1	1	1
7	1	1	1

↑ Canonical
Storage. ⑧ bits

Logic Expression

$$F = \overline{X} \cdot \overline{Y} \cdot Z + X \cdot \overline{Y} \cdot \overline{Z} + X \cdot \overline{Y} \cdot Z$$

$$\overbrace{X \cdot Y \cdot \overline{Z}}^{\text{SOP}} + \overbrace{X \cdot Y \cdot Z}^{\text{SOP}}$$

→ 2^{16} bit 64 bit adder
 $64 + 64 = 128$

$$2^{128} \text{ bits} \approx 2^{120} = 10^{36} \text{ bits}$$



Min Terms

Truth Table

X Y Z	F
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

0
1
2
3
4
5
6
7

↑

$\bar{x} \cdot \bar{y} \cdot z$


term.

Min

$\bar{x} \bar{y} z$

$$= \sum 1, 4, 5, 6, 7$$

m_1, m_4, m_5, m_6, m_2

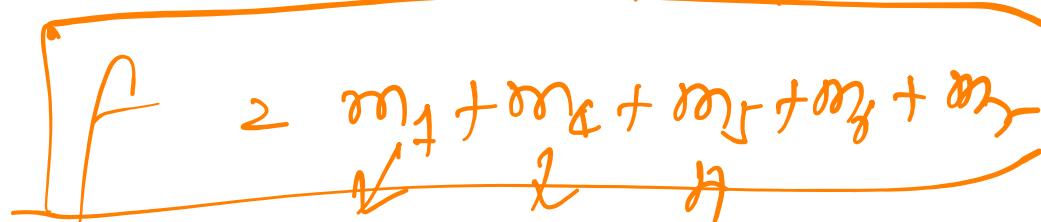

$\bar{x} \bar{y} z$ $x \bar{y} z$ $x \bar{y} \bar{z}$

SOP



$$\bar{x} + y + z$$

$$x + \bar{y} + z$$

$$x + y + \bar{z}$$

Max Terms

$$F = \frac{\bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z}{x+y+z}$$

Truth Table

X	Y	Z	F
0	0	0	0
1	0	1	1
2	1	0	0
3	0	1	0
4	1	0	1
5	1	1	1
6	1	0	1
7	1	1	1

$$F: \underline{x+y+2} F = C$$



$$M_0 \cdot M_2 \cdot M_3 \rightarrow$$

$$F: (x+y+z) \cdot (x+\bar{y}+z) \cdot (x+y+\bar{z})$$

M₀

POS

M₂ M₃

'Unique'

(5) (3)



Thank You

