

Logic Optimization

Virendra Singh

Professor

Computer Architecture and Dependable Systems Lab

Department of Computer Science & Engineering, and

Department of Electrical Engineering

Indian Institute of Technology Bombay

<http://www.cse.iitb.ac.in/~viren/>

E-mail: viren@{cse, ee}.iitb.ac.in

CS-230: Digital Logic Design & Computer Architecture



Lecture 9 (24 January 2022)

CADSL

Representations

- ① Truth Table
- ② Sum of min terms
- ③ Product of Max terms

UNIQUE
↑
Comoni
cat.

Graphical.

- ④ Binary Decision Diagram (BDD) ← Canonical
 - ⑤ Reed Muller Representation - canonical.
= (AND and XOR)
 - ⑥ And Inverter Graph (AIG) ↗ not canonical
ABC. ↑
 - ⑦ SOP
 - ⑧ POS ↗ non-canonical
 - ⑨ Hybrid 2
- CADSL



Function Minimization

$$\left\{ \begin{array}{l} \text{SOP} \rightarrow \text{2level.} \\ \text{POS} \Rightarrow \text{2level} \end{array} \right. \quad \begin{array}{l} \text{AND} \rightarrow \text{OR} \oplus \\ \text{OR} \rightarrow \text{AND} \oplus \end{array} \quad \begin{array}{l} \text{NAND-NAND} \\ \text{NOR-NOR} \end{array}$$

minimize \rightarrow Boolean Algebra ✓

\Rightarrow Not scalable approach]

✓ Automatic ✓


Algorithmic approach.

① Graphical Method. (K-Map)

② Tabular Method. (QM.)



NAND

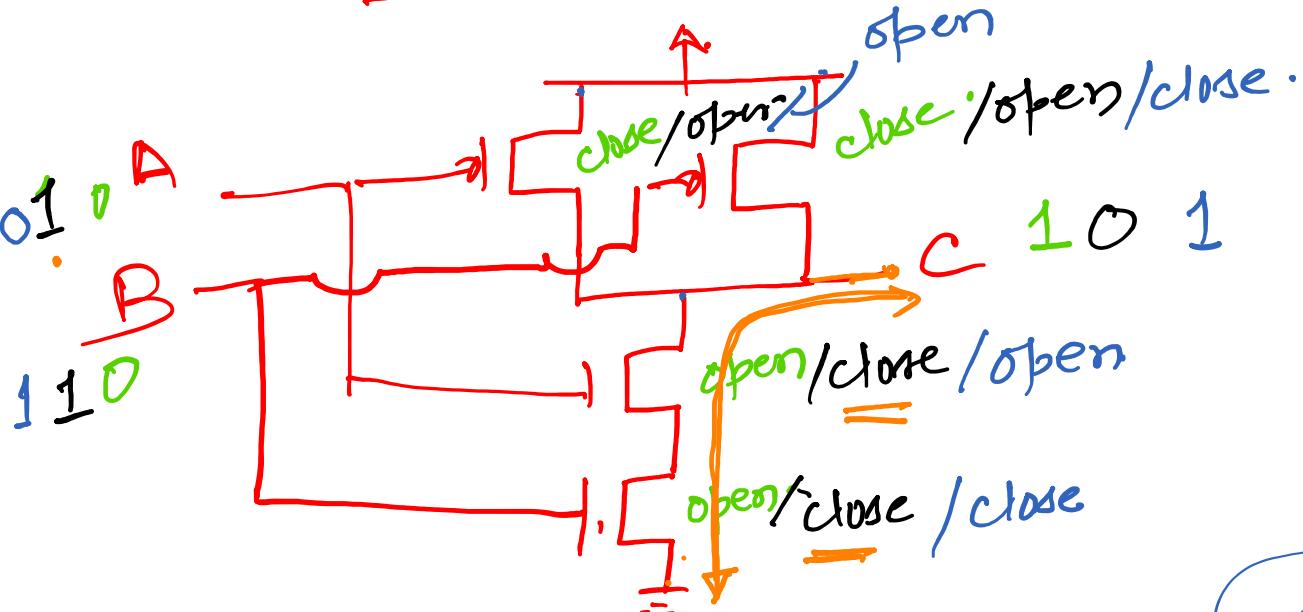

0 0	-	1
0 1	-	1
1 0	-	1
1 1	-	0

NAND =

Delay.

[delay of one switch is τ]

Delay of 2 input

NAND is $\underline{2\tau}$

for N input $\underline{\text{NAND}} = \underline{N\tau}$



4 switches

$N \text{ input} = 2N$
switches
transistors



COST of N input NAND = $2N$ ·
delay of N input-NAND = $N \tau_c$.

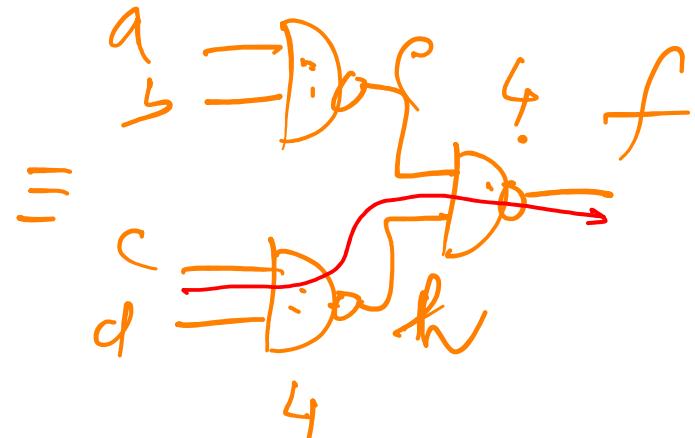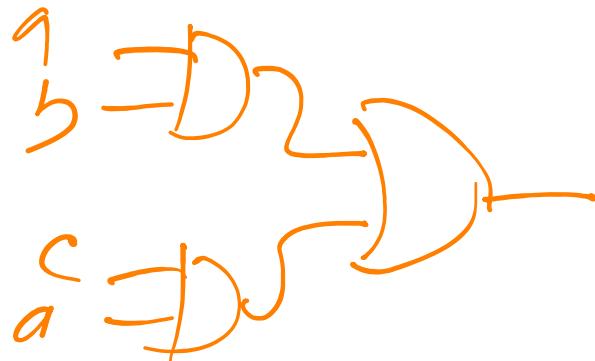
$$f(a, b, c, d) = \underline{\overline{ab} + \overline{cd}} \quad 4$$



COST = $2 \times \# \text{ literals} + 2 \times \# \text{ product terms}$ ·



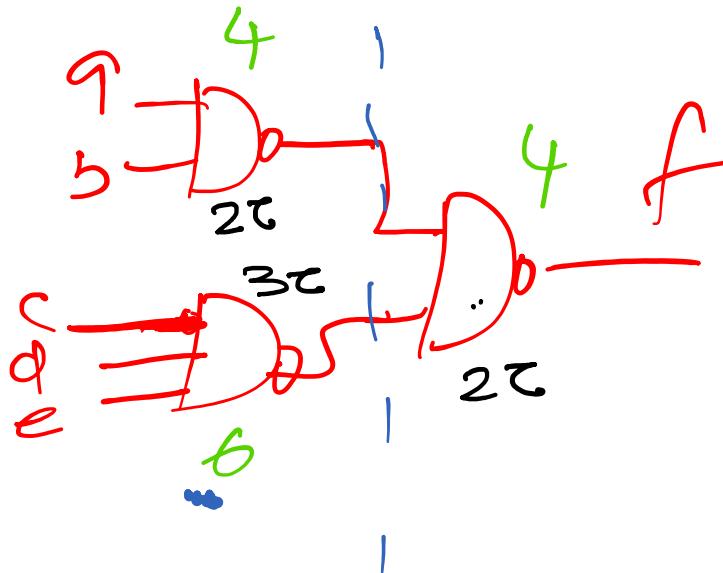
$$f(a,b,c,d,e) = \underline{ab} + \underline{cde}$$



delay = Max delay of first level + delay of second level
~~= {10, 2τ}~~ + $\max\{2\tau, 3\tau\} + 2\tau = 5\tau$

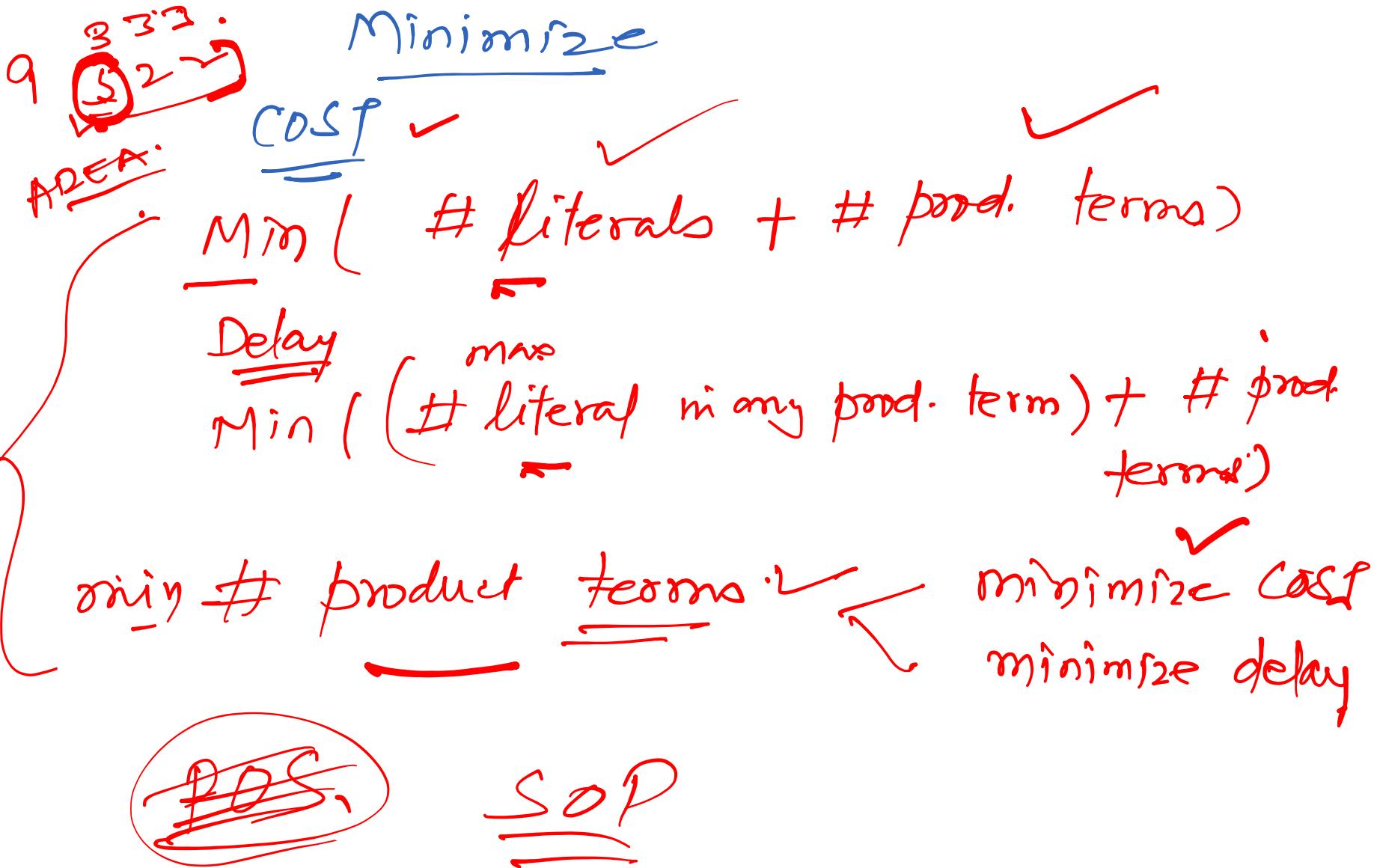(Max literals in any prod. term + # prod. term)





Logic Minimization

- Generally means
 - In SOP form:
 - Minimize number of products (reduce gates) and
 - Minimize literals (reduce gate inputs)
 - In POS form:
 - Minimize number of sums (reduce gates) and
 - Minimize literals (reduce gate inputs)

$$\begin{array}{l} \overbrace{\begin{array}{l} a=1 \\ \& b=1 \end{array}}^{\text{impllicants}} \Rightarrow f=1 \quad f(a,b) \\ \text{impllicants} \end{array}$$

8

a	b	
0	0	0
0	1	0
1	0	0
1	1	1

8



Product or Implicant or Cube

- Any set of literals ANDed together.
- Minterm is a special case where all variables are present. It is the largest product.
- A minterm is also called a 0-implicant of 0-cube.
- A (1-implicant) or 1-cube is a product with one variable eliminated:

- Obtained by combining two adjacent 0-cubes

$$\checkmark \overline{ABCD} + \checkmark \overline{ABC} \cdot \overline{D} = ABC(\overline{D} + \overline{\overline{D}}) = ABC$$

$ABC \rightarrow f$



Function Minimization


$$\begin{aligned}f(a,b) &= ab + a\bar{b} \\&= a \cdot \underbrace{(b + \bar{b})}_{1} = a\end{aligned}$$



Graphical Method: Karnaugh Map

Maurice Karnaugh

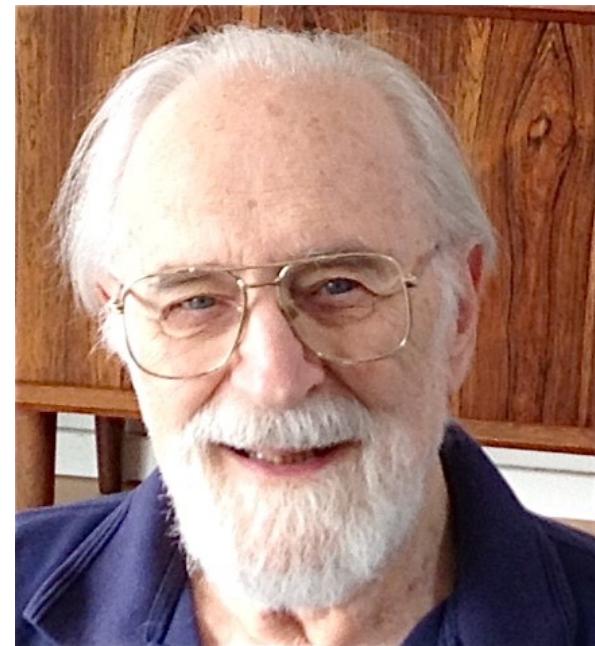- American Physicist
- Bell Lab (1952 – 66)
- Developed K-Map in 1954



Maurice Karnaugh
Born: 4 October 1924

Karnaugh, Maurice (November 1953), ["The Map Method for Synthesis of Combinational Logic Circuits"](#). [Transactions of the American Institute of Electrical Engineers, Part I: Communication and Electronics](#). 72(5): 593–599



Function Minimization: K-Map

$$f(a,b) = \underline{ab+a\bar{b}} = a \cdot (\underline{b+\bar{b}}) = a \quad a \rightarrow f$$

$$\Rightarrow ab + a\bar{b} \rightarrow a \leq$$

a	b	f(a,b)
0	0	1
0	1	0
1	0	0
1	1	1

$$f(\underline{a}) = a \\ f(\bar{a}) = \bar{a}$$

$$a \quad \begin{array}{|c|c|}\hline 0 & 1 \\ \hline 1 & 1 \\ \hline \end{array} \quad f=1$$

a	b	c
0	0	1
0	1	0
1	0	0
1	1	1


$$a \quad \begin{array}{|c|c|c|c|}\hline b & 0 & 1 & \\ \hline 0 & 1 & 1 & 0 \\ \hline 1 & 0 & 0 & 0 \\ \hline \end{array} \quad f(a,b) = \bar{b}$$

$$ab \quad \begin{array}{|c|c|c|c|}\hline b \backslash a & 00 & 01 & 11 & 10 \\ \hline 00 & 1 & 0 & 0 & 1 \\ \hline 01 & 0 & 1 & 0 & 1 \\ \hline 11 & 0 & 0 & 1 & 1 \\ \hline 10 & 1 & 1 & 1 & 0 \\ \hline \end{array}$$

$$f(a,b) = \bar{b}$$



Function Minimization: K-Map

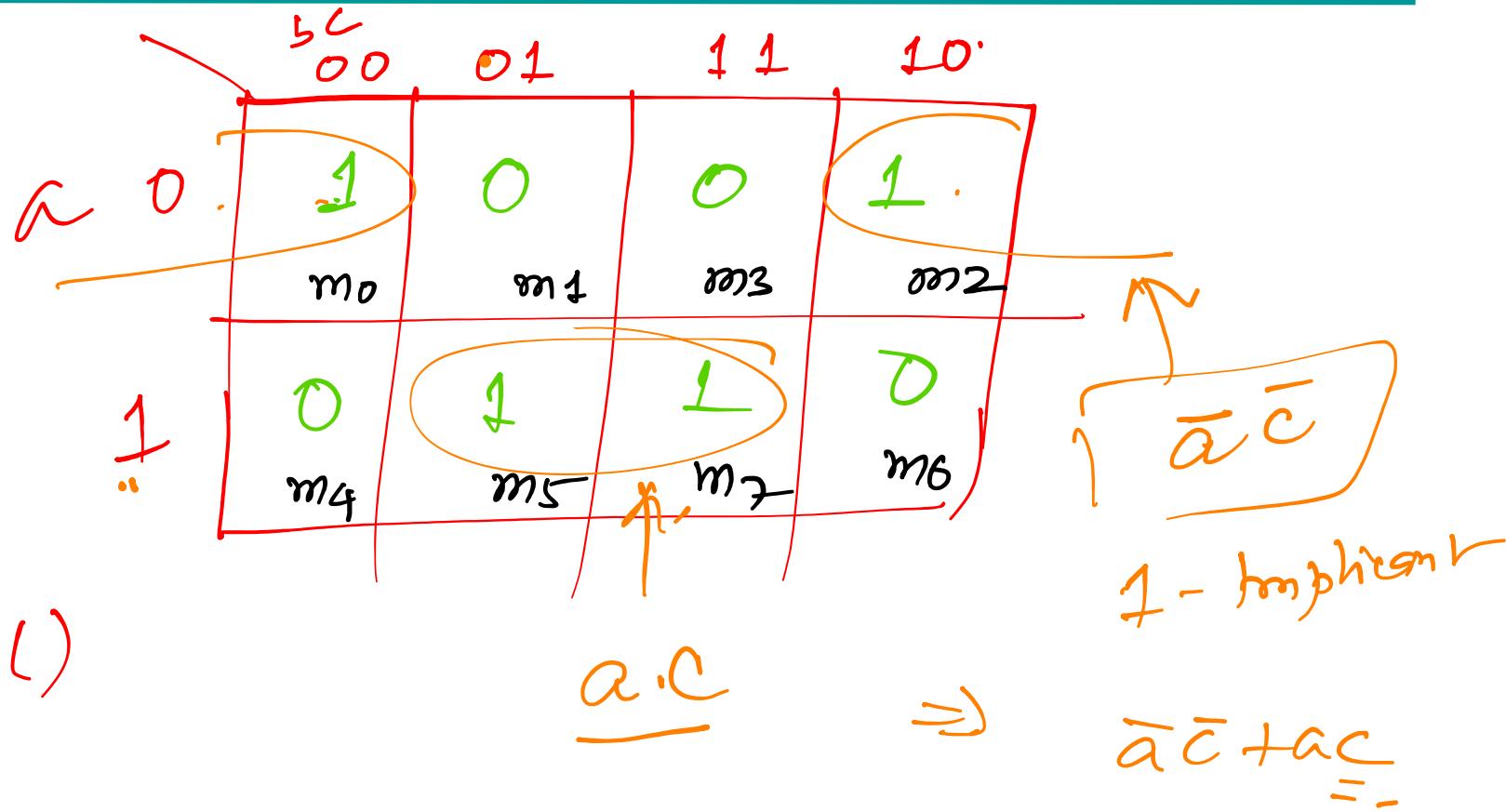

$f(a,b,c)$

$a \cdot c$


\Rightarrow

1 - Implicant


$\bar{a} \bar{c} + a c$



Function Minimization: K-Map

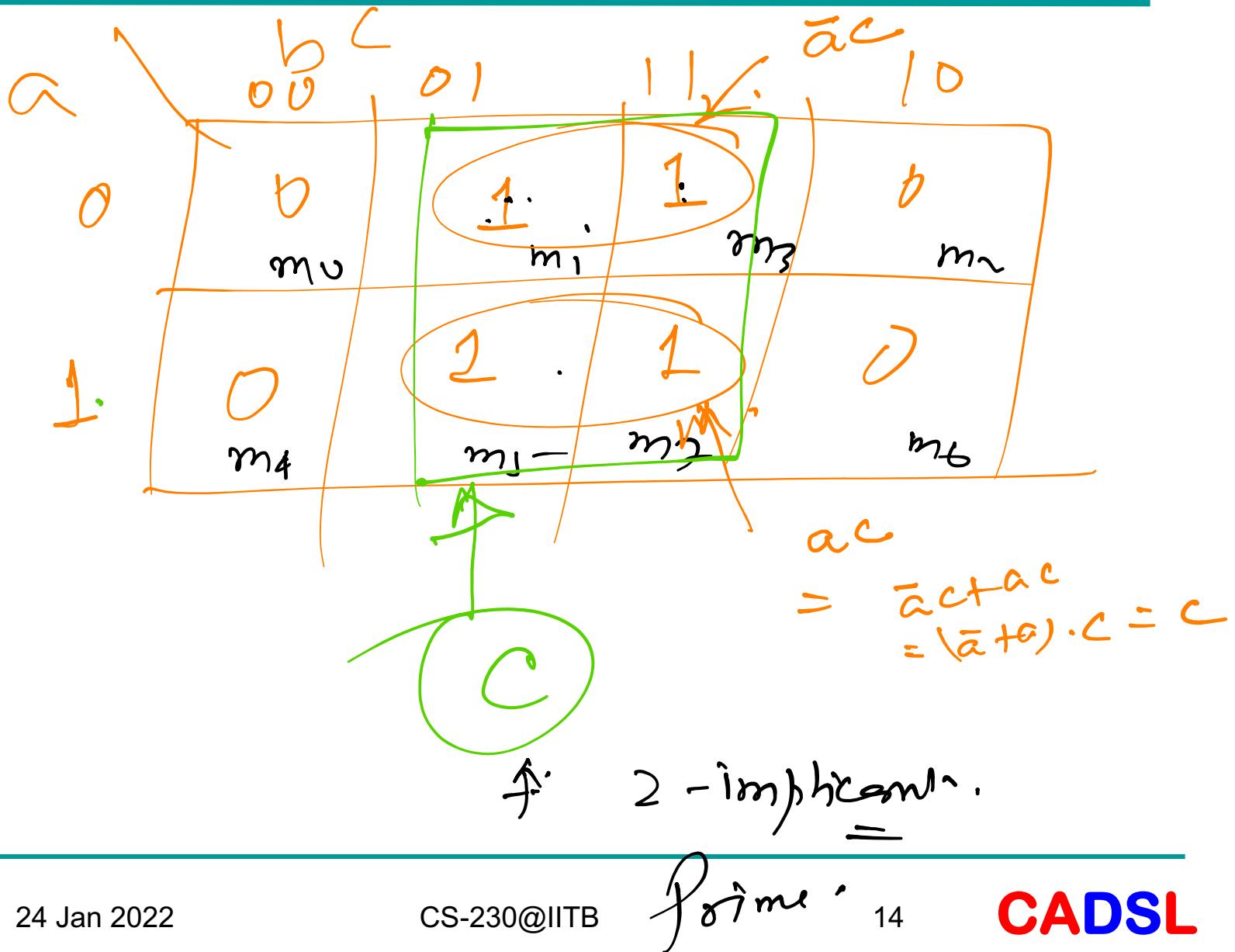


Function Minimization: K-Map

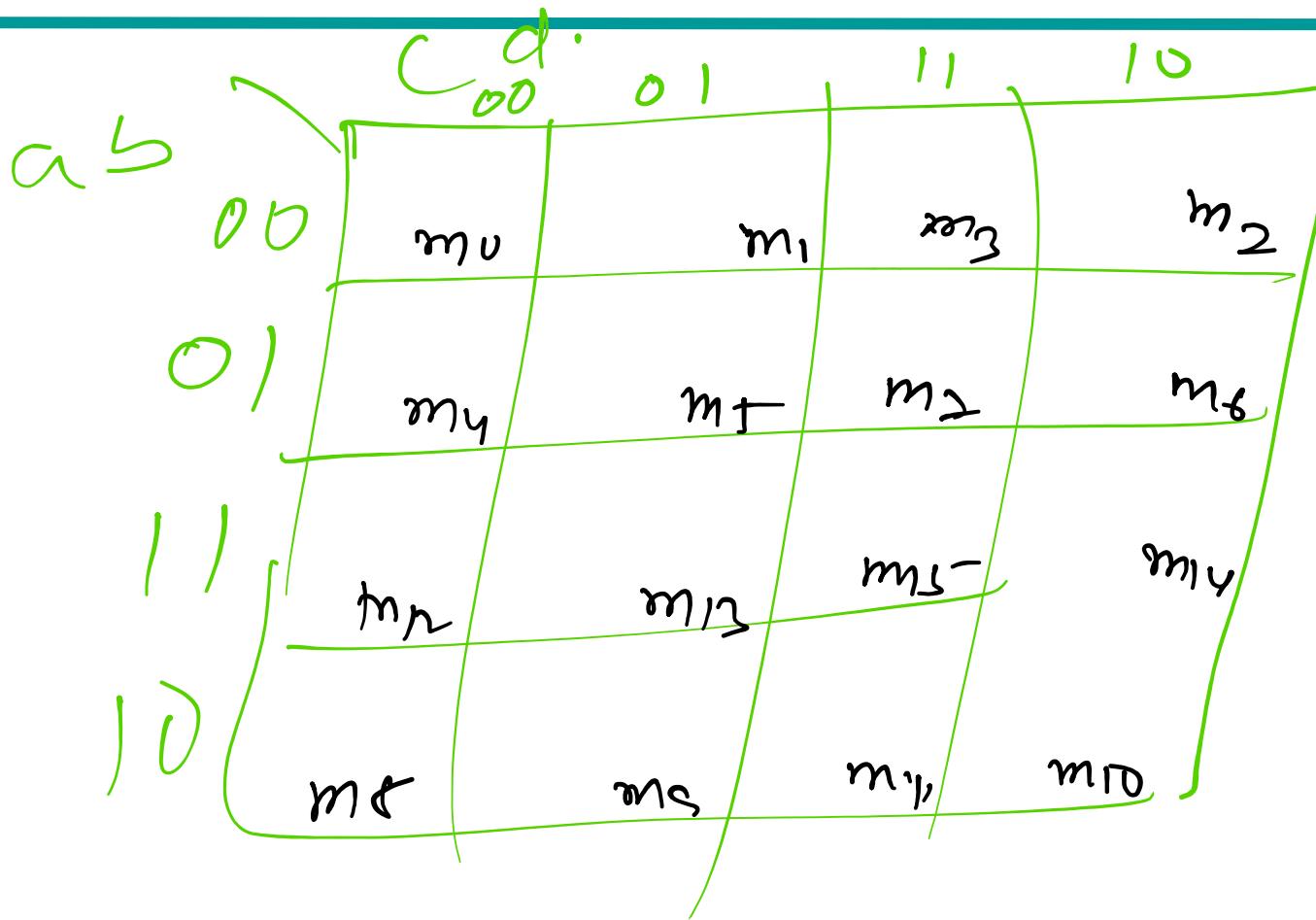


PRIME IMPLIC.



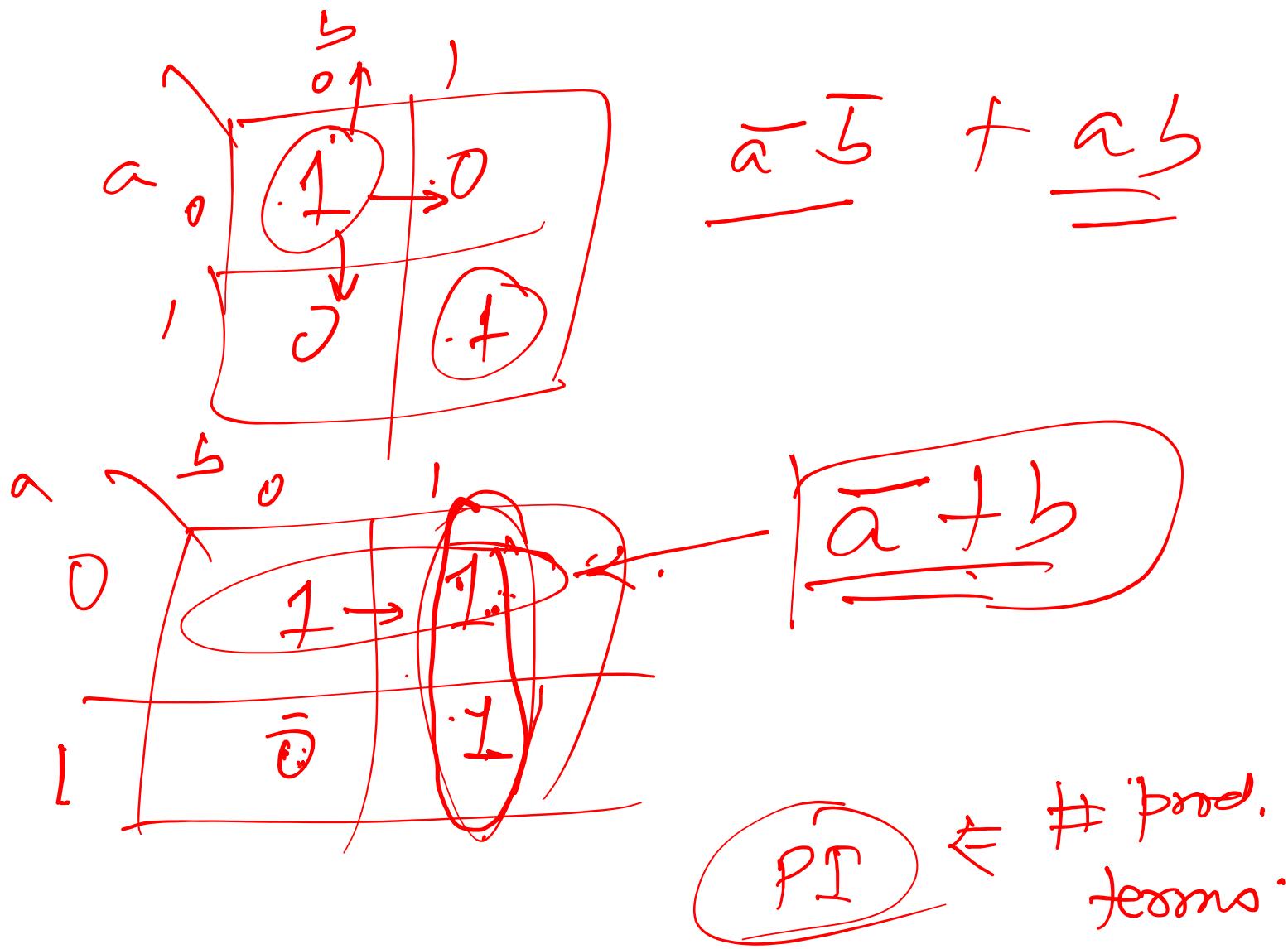

Cubes (Implicants) of 4 Variables

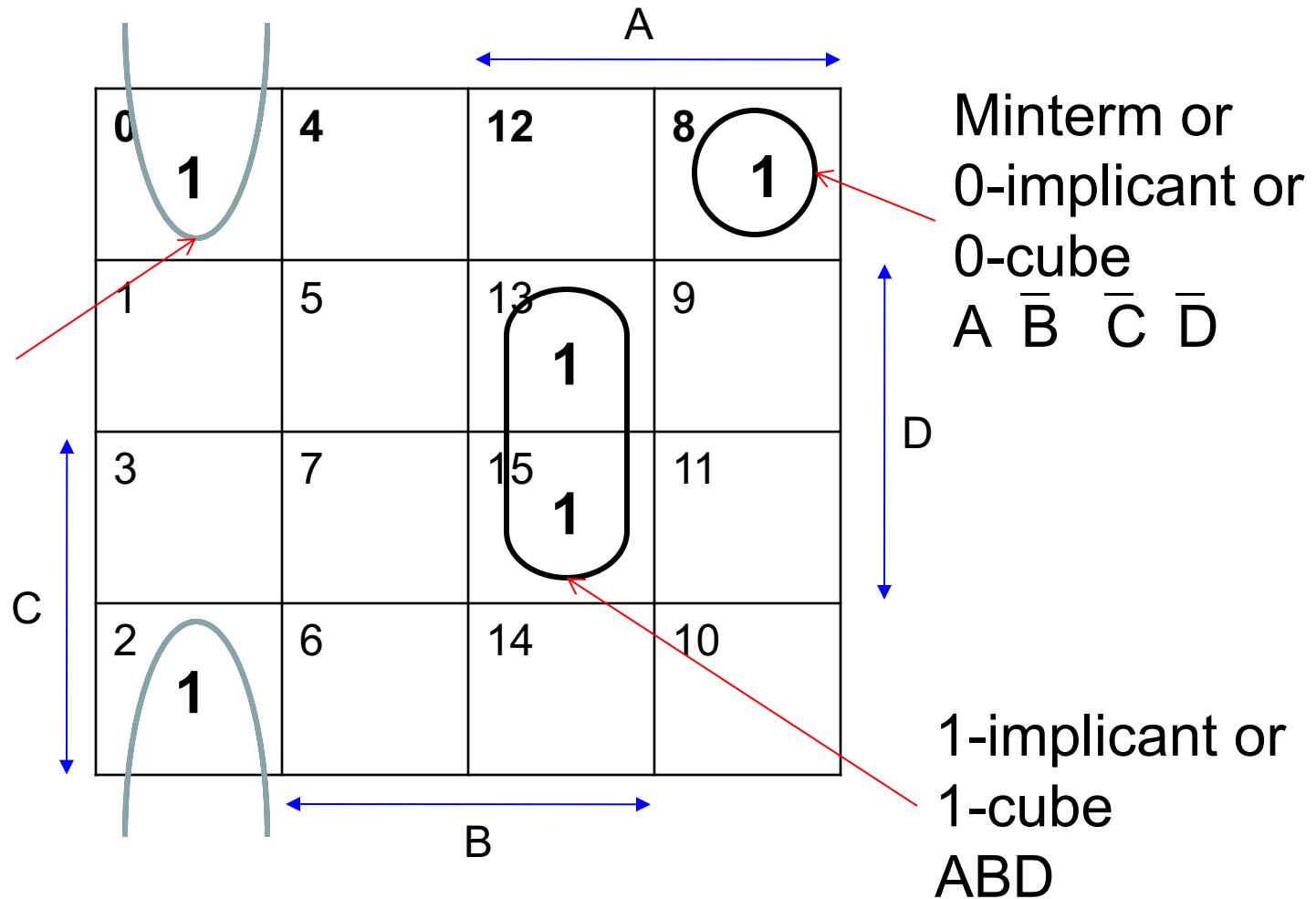

Thank You

